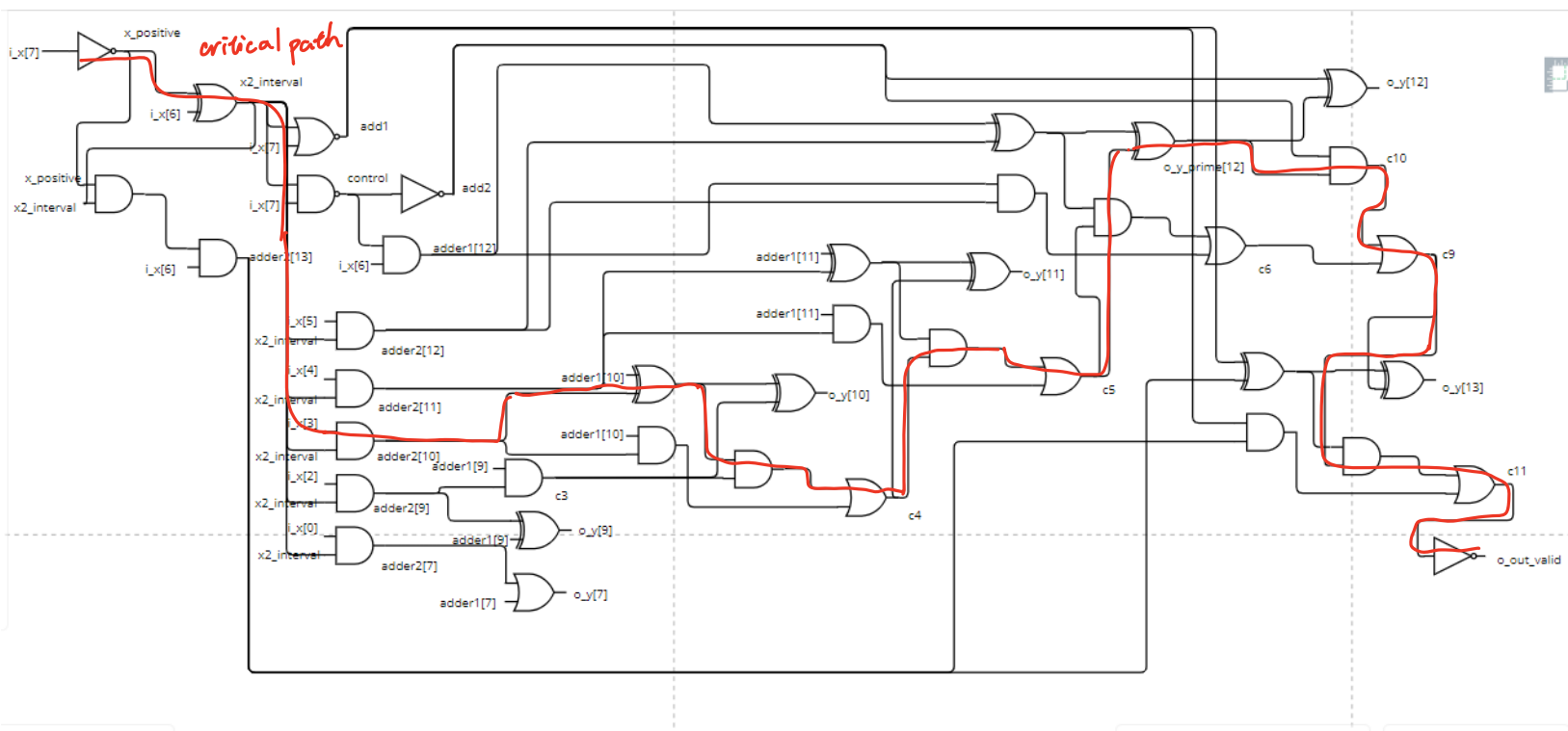



(a) the minimum cycle time is 7.4ns

Simulation finished	
Summary	
Clock cycle:	7.4 ns
Number of transistors:	210
Total execution cycle:	255
Approximation Error Score:	662950.0
Performance Score:	396270.0

(b)



(c)

 

use piecewise linear approximation (4 segments)

- slope: 2^{-4} ($y = 2^{-4}x + \underline{2^{-2}} + \underline{2^{-1}}$) $2 \leq x < 4$ ^{add1}

- slope: $2^{-3} + 2^{-4}$ ($y = 2^{-4}x + 2^{-3}x + \underline{2^{-1}}$) $0 \leq x < 2$

- slope: $2^{-3} + 2^{-4}$ ($y = 2^{-4}x + 2^{-3}x + \underline{2^{-1}}$) $-2 < x < 0$ ^{add2}

- slope: 2^{-4} ($y = 2^{-4}x$) $-4 < x \leq -2$

(1) for $x \geq 0$, $x_positive = 1$, $o_y[14] = x_positive = 1$ ($y \geq 0.5$)

(2) for $-2 < x < 2$, $x2_interval = 1$, indicates that the slope will be $2^{-3} + 2^{-4}$ (else slope = 2^{-4})

(3) for $2 \leq x < 4$ ($x_positive = 1$ and $x2_interval = 0$), y need to add 2^{-2} (add1 = 1, else add1 = 0)

(4) for $-2 < x < 0$ ($x_positive = 0$ and $x2_interval = 1$), y need to add 2^{-1} (add2 = 1, else add2 = 0)

$\therefore x < 0$ is 2's complement \therefore for $-2 < x < 0$, the equation $y = 2^{-4}x + 2^{-3}x + 2^{-1}$, x only use $i_x[5:0]$

and we use control to represent $x > 0$ or $x \leq -2$ (x can use $i_x[6:0]$)

(5) we use adder1[15:0] to represent $2^{-4} \cdot x$. adder2[15:0] to represent $2^{-3}x$

(6) according to different condition, use (1) ~ (5), half adder, full adder to complete the circuit *

To improve the critical path and the number of transistors, we use NAND, NOR gates

instead of AND, OR gates. Besides, I sacrifice the accuracy to improve both the critical path

and the number of transistors. (give up using full adder in LSB calculation)

HAI ha1($c1$, $o_y[1]$, adder1[1], adder2[1])

FA1 fa2($c2$, $o_y[8]$, adder1[8], adder2[8], $c1$)

FA1 fa3($c3$, $o_y[9]$, adder1[9], adder2[9], $c2$)

↓ after trade-off with accuracy

OR2 or5($o_y[1]$, adder1[1], adder2[1])

assign $o_y[8] = \text{adder1}[8]$

HAI ha2($c3$, $o_y[9]$, adder1[9], adder2[9]) *

Carry lookahead Adder

(used in $2^{-3}x + 2^{-4}x$)

more area, less delay


after trade-off
between area and speed
↔

Ripple Carry Adder

(used in $2^{-3}x + 2^{-4}x$)

less area, more delay *

original design

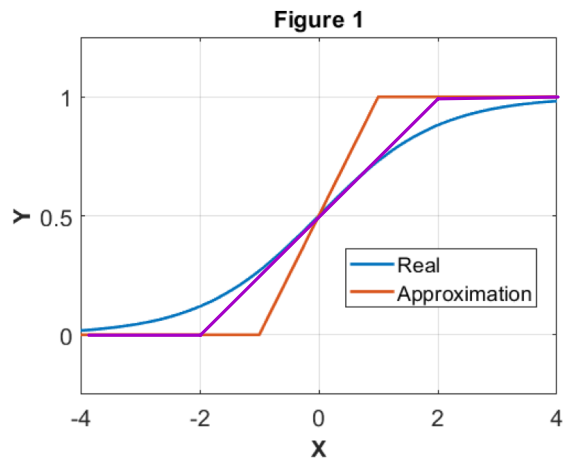

three segments

higher approximation error

lower critical path and number of transistors #